

Preparation branchement Leds ...

Materiels

1. 2 leds
2. 2 resistances
3. la soudure
4. la gaine thermo
5. 1 mini interrupteurs

schema Principe

1 Led



2 Leds



Schema cablage

1 led




2 leds




2 leds sur Tinkercad

Led Clignotante

schema principe

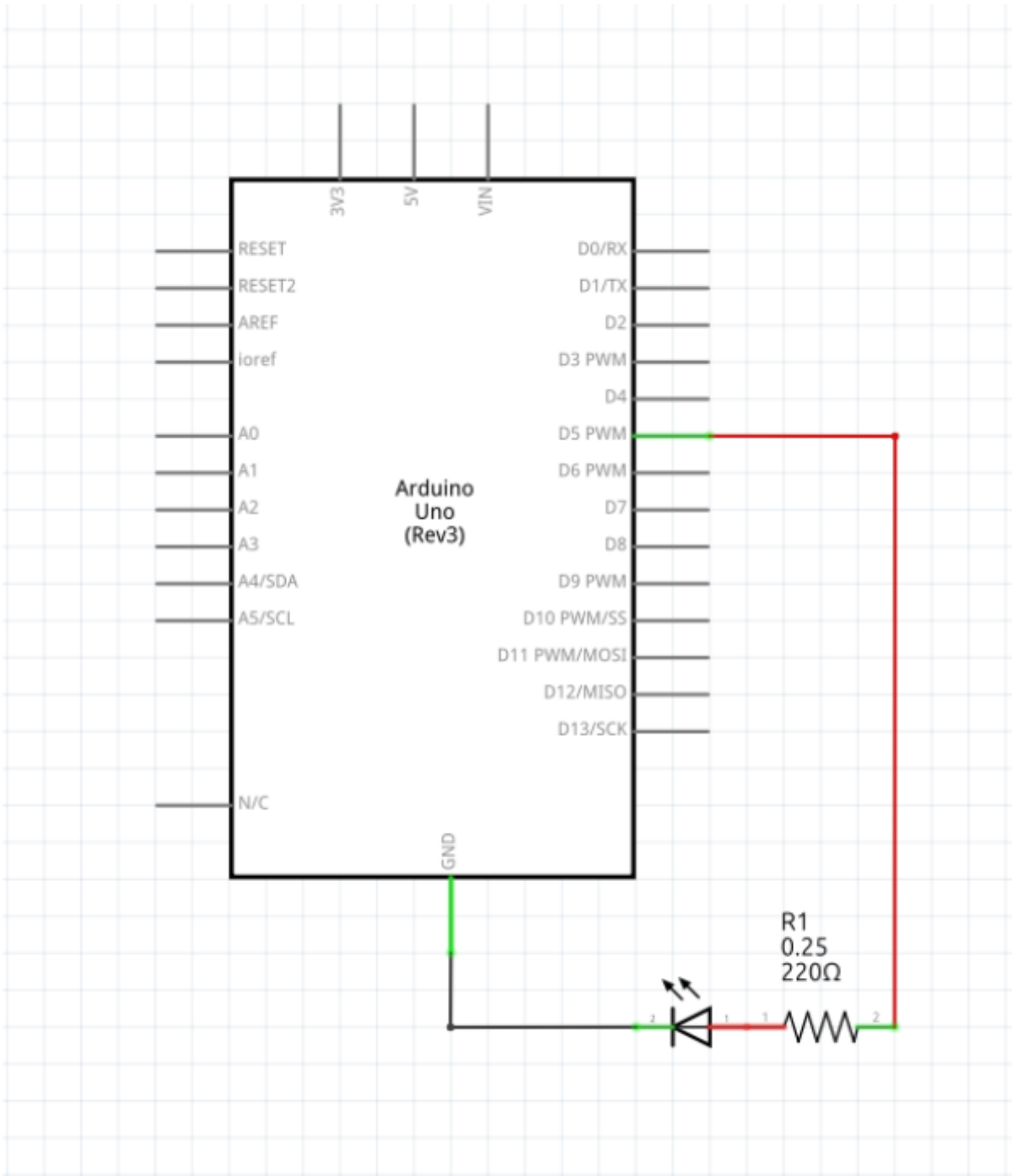

Schema cablage

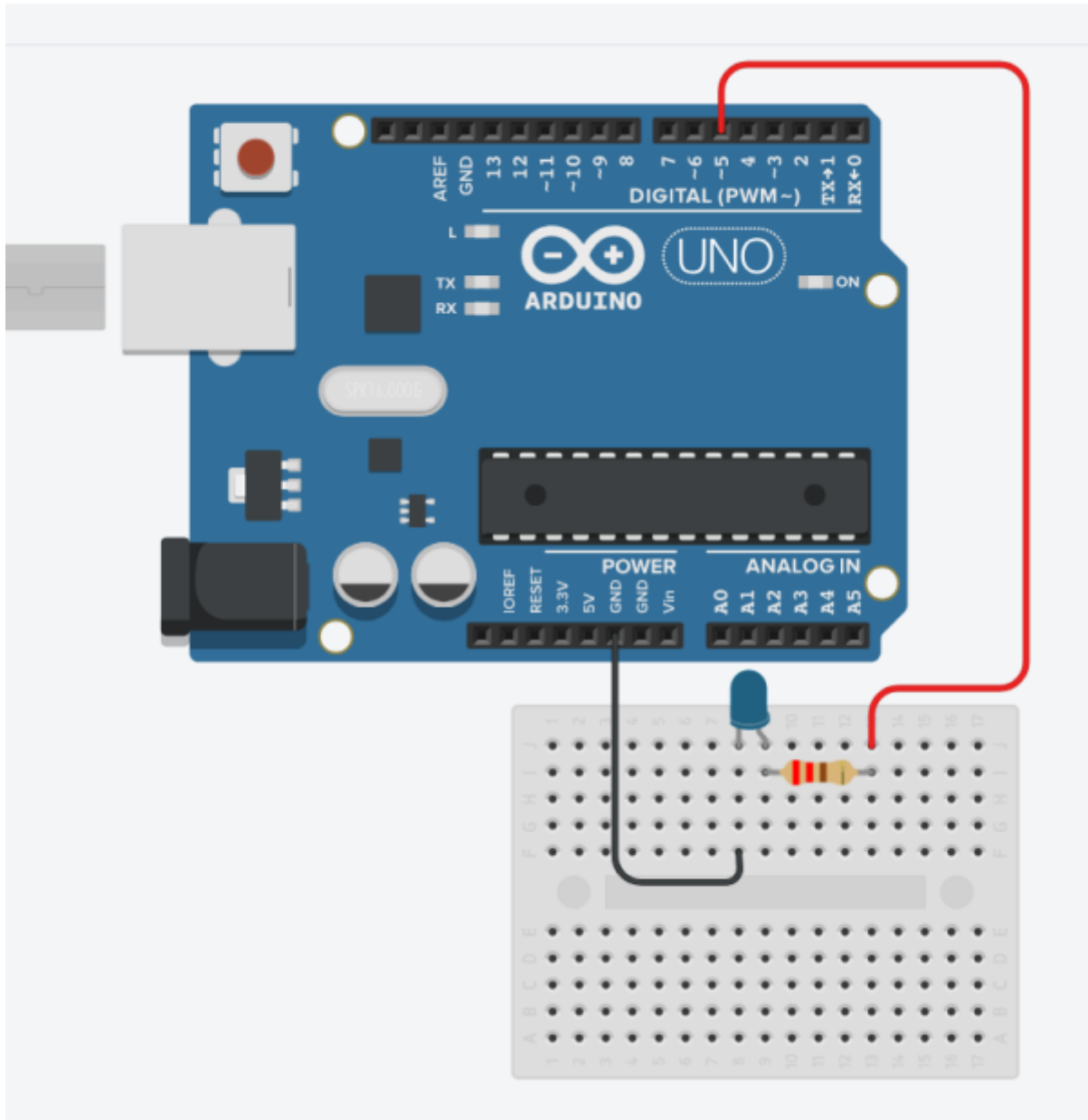

Code

mode texte

[ledclignote.ino](#)

```
// C++ code
//
void setup()
{
  pinMode(5, OUTPUT);
}

void loop()
{
  analogWrite(5, 1);
}
```

```
delay(1000); // Wait for 1000 millisecond(s)  
analogWrite(5, 0);  
delay(1000); // Wait for 1000 millisecond(s)  
}
```

mode bloc



From: <https://magenealogie.chanterie37.fr/www/fablab37110/> - Castel'Lab le Fablab MJC de Château-Renault

Permanent link: <https://magenealogie.chanterie37.fr/www/fablab37110/doku.php?id=start:jeunes:prepa:branceleds&rev=1759346931>

Last update: 2025/10/01 21:28

